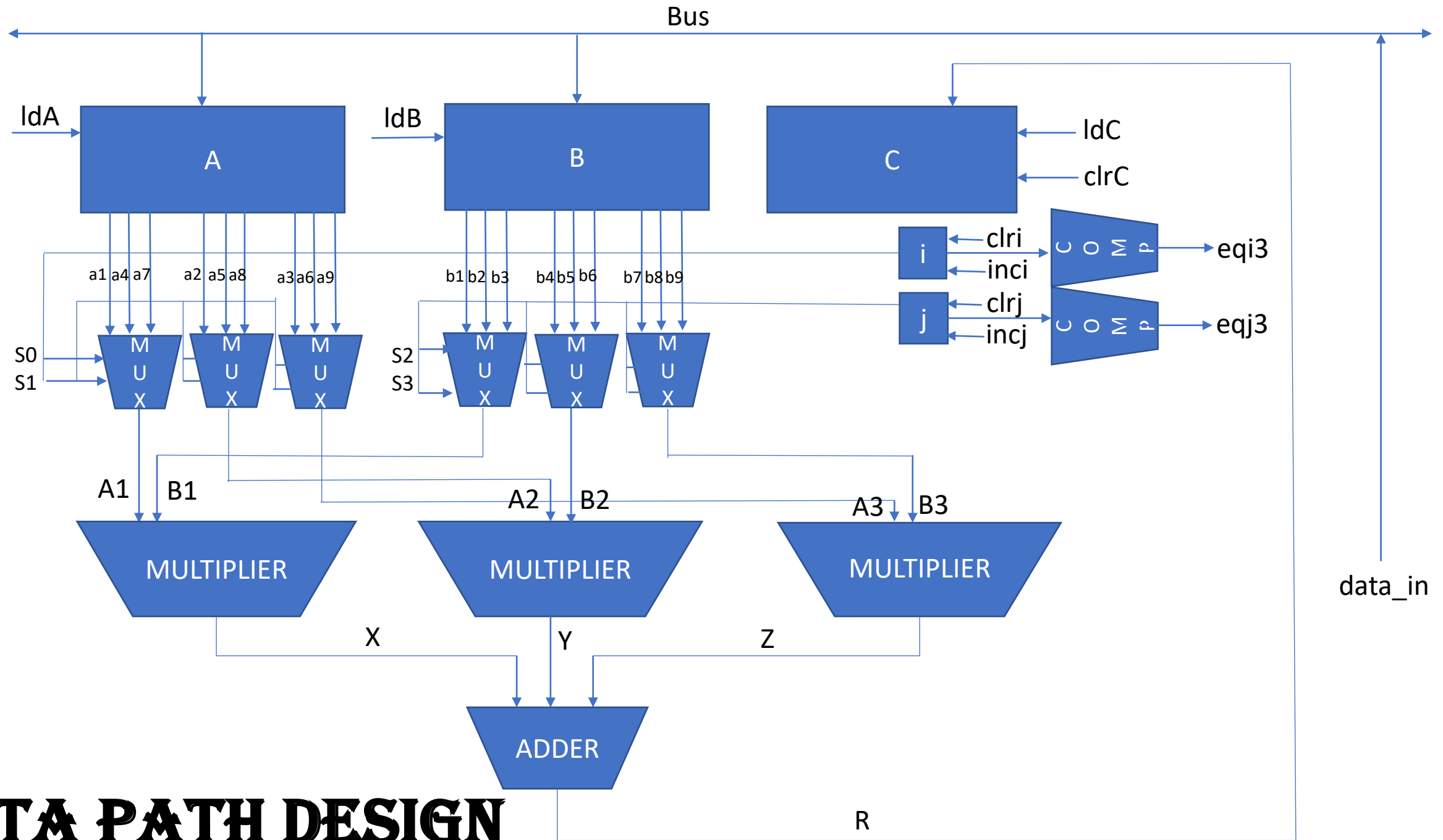


3 X 3 MATRIX MULTIPLIER



DESCRIPTION:

- ❑ Implemented the **Datapath and Controller Hardware Design** of **3 x 3 Matrix Multiplier** in **Verilog HDL**.
- ❑ The inputs of the design are **two 3 x 3 matrices** consisting of **nine 8-bit numbers** and the processed output is a **3 x 3 matrix** consisting of **nine 16-bit numbers**.
- ❑ The design of the Datapath includes **two 72 bit registers** to store the input matrices and **one 144 bit register** to store the output matrix.
- ❑ The input data is fed to the hardware through the **bus** in the form of **binary** and is stored in the required registers.
- ❑ The inputs are processed accordingly using **three MUXes, three Multipliers, and an Adder** to implement the Matrix Multiplication (using a conventional matrix multiplication algorithm) on the two inputs and the processed output is stored in the required register.
- ❑ The Controller design consists an **FSM** of **five states**, So **three flipflops** are needed to implement those five states in FSM.
- ❑ A **clock signal** of required frequency is also being fed to the Datapath and Controller.




DATA PATH DESIGN

CONTROL PATH DESIGN

 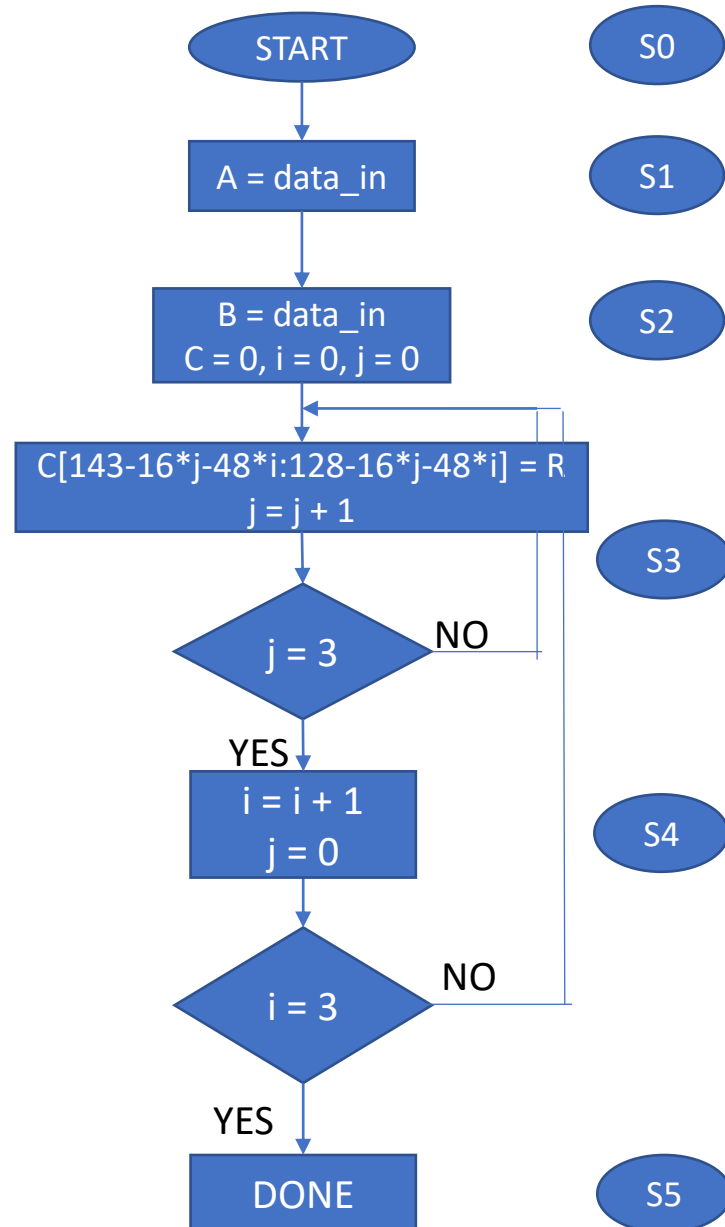

COMPLETE DESIGN

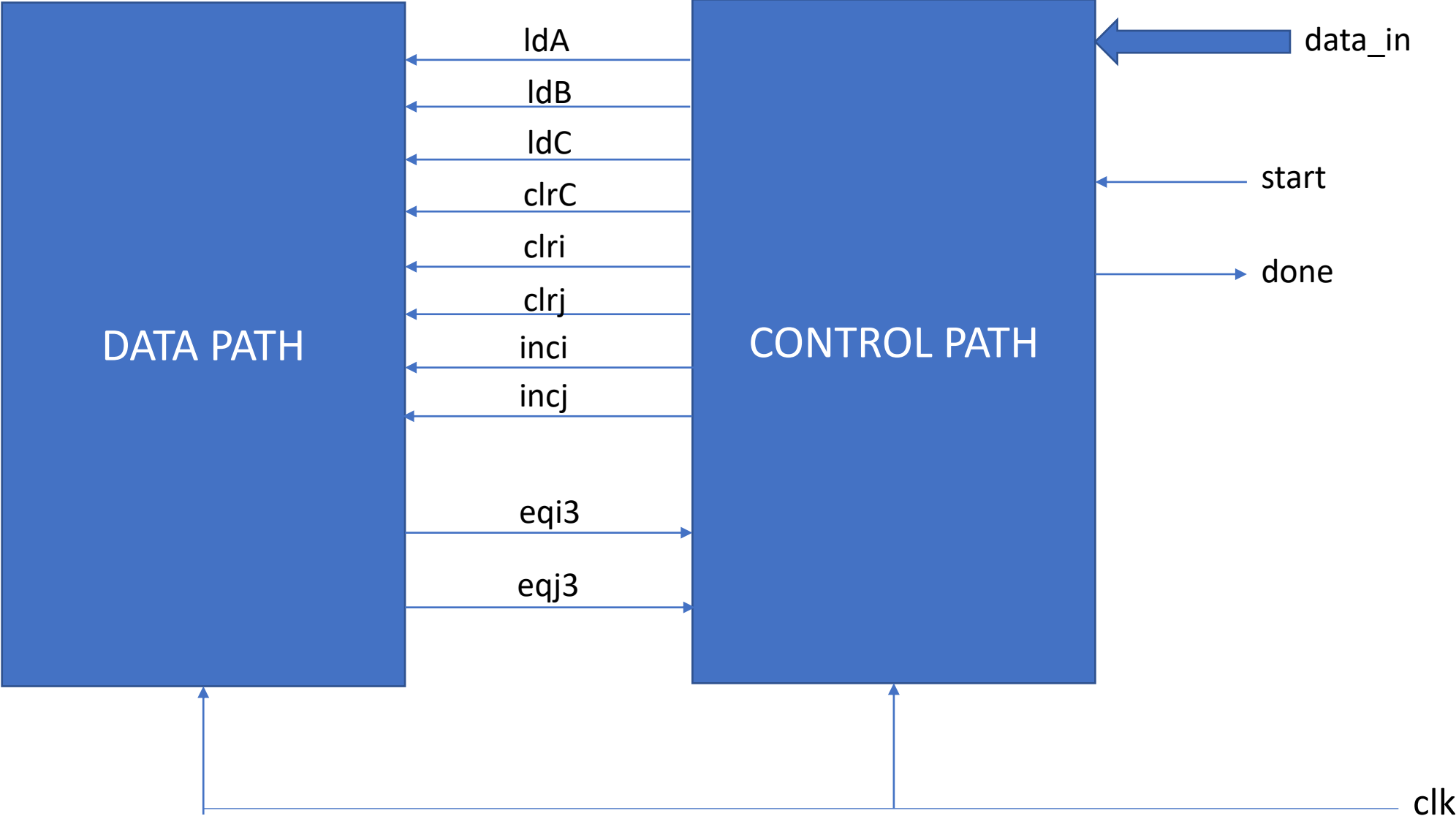

VERILOG CODE FOR DATAPATH DESIGN

```
module MatrixMultiplier_datapath (eqi3, eqj3, ldA, ldB, ldC, clri, clrj, inci, incj, data_in, clk);
    input ldA, ldB, ldC, clri, clrj, inci, incj, clk;
    input [71:0] data_in;
    output reg eqi3, eqj3;
    reg [71:0] A, B;
    reg [143:0] C;
    reg [1:0] i, j;
    wire [7:0] A1, A2, A3, B1, B2, B3;
    wire [15:0] X, Y, Z, R

    PIPO1 A (A, data_in, ldA, clk);
    PIPO1 B (B, data_in, ldB, clk);
    PIPO2 C (C, C[143-16*j-48*i:128-16*j-48*i], R, ldC, clk);
    PIPO3 I (i, clri, inci, clk);
    PIPO3 J (j, clrj, incj, clk);
    MUX MUX_1 (A1, A[71:64], A[57:40], A[23:16], i);
    MUX MUX_2 (A2, A[63:56], A[39:32], A[15:8], i);
    MUX MUX_3 (A3, A[55:48], A[31:24], A[7:0], i);
    MUX MUX_4 (B1, B[71:64], B[63:56], B[55:48], j);
    MUX MUX_5 (B2, B[47:40], B[39:32], B[31:24], j);
    MUX MUX_6 (B3, B[23:16], B[15:8], B[7:0], j);
    MULTIPLY MUL_1 (X, A1, B1);
    MULTIPLY MUL_2 (Y, A2, B2);
    MULTIPLY MUL_3 (Z, A3, B3);
    ADDER ADD (R, X, Y, Z);
    COMPARE COMP (eqi3, i);
    COMPARE COMP (eqj3, j);
endmodule
```

```
module PIPO1 (d_out, d_in, ld, clk);  
    input [71:0] d_in;  
    input ld, clk;  
    output reg [71:0] d_out;  
    always @(posedge clk)  
        if (ld) dout <= din;  
endmodule
```

```
module PIPO2 (d_out, d_in, ld, clk);  
    input [15:0] d_in;  
    input ld, clk;  
    output reg [15:0] d_out;  
    always @(posedge clk)  
        if (ld) d_out <= d_in;  
endmodule
```

```
module PIPO3 (d_out, clr, inc, clk);  
    input clr, inc, clk;  
    output reg [1:0] d_out;  
    always @(posedge clk)  
        if (clr) d_out <= 2'b0;  
        else if (inc) d_out <= d_out + 1;  
endmodule
```

```
module MUX (out, in0, in1, in2, sel);  
    input [7:0] in0, in1, in2;  
    input [1:0] sel;  
    output [7:0] out;  
    if (sel = 0) assign out = in0;  
    if (sel = 1) assign out = in1;  
    if (sel = 2) assign out = in2;  
endmodule
```

```
module MULTIPLY (out, in1, in2);  
    input [7:0] in1, in2;  
    output [15:0] out;  
    always @(*)  
        out = in1 * in2;  
endmodule
```

```
module ADDER (out, in1, in2, in3);  
    input [15:0] in1, in2;  
    output reg [15:0] out;  
    always @(*)  
        out = in1 + in2 + in3;  
endmodule
```

```
module COMPARE (eq, data);  
    input [1:0] data1, data2;  
    output eq;  
    assign eq = data == 3;  
endmodule
```

VERILOG CODE FOR CONTROLLER DESIGN

```
module controller (ldA, ldB, ldC, clri, clrj, inci, incj, done, clk, eqi3, eqj3, start);  
    input clk, eqi3, eqj3, start;  
    output reg ldA, ldB, ldC, clri, clrj, inci, incj, done;  
    reg [3:0] state;  
    parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010, S3 = 3'b011, S4 = 3'b100, S5 = 3'b101;  
    always @(posedge clk)  
        begin  
            case (state)  
                S0 : if (start) state <= S1;  
                S1 : state <= S2;  
                S2 : state <= S3;  
                S3 : #2 if(eqj3) state <= S4;  
                     else state <= S3;  
                S4 : #2 if(eqi3) state <= S5;  
                     else state <= S3;  
                default: state <= S0;  
            endcase  
        end  
end
```



```
always @(state)
begin
    case (state)
        S0 : begin #1 ldA = 0; ldB = 0; ldC = 0; clri = 0; clrj = 0; inci = 0; incj = 0; end
        S1 : begin #1 ldA = 1; end
        S2 : begin #1 ldA = 0; ldB = 1; clri = 1; clrj = 1; end
        S3 : begin #1 ldB = 0; ldC = 1; incj = 1; clrj = 0; clri = 0; end
        S4 : begin #1 incj = 0; clrj = 1; inci = 1; end
        S5 : begin #1 done = 1; ldC = 0; inci = 0; clri = 0; clrj = 0; end
        default: begin #1 1 ldA = 0; ldB = 0; ldC = 0; clri = 0; clrj = 0; inci = 0; incj = 0; end
    endcase
end
endmodule
```

VERILOG CODE FOR TESTBENCH

```
module MatrixMultiplier_test;
    reg [71:0] data_in;
    reg clk, start, done;
    reg [71:0] A, B;
    reg [143:0] C;
    reg [1:0] i, j;
    MatrixMultiplier_datapath DP (eqi3, eqj3, ldA, ldB, ldC, clrC, clri, clrj, inci, incj, data_in, clk);
    controller CONTROLLER (ldA, ldB, ldC, clrC, clri, clrj, inci, incj, done, clk, eqi3, eqj3, start);
    initial
        begin
            clk = 1'b0;
            #3 start = 1'b1;
            #1000 $finish;
        end
    always #5 clk = ~clk;
    initial
        begin
            #12 data_in = [1:2:3:4:5:6:7:8:9];
            #10 data_in = [2:3:4:5:6:7:8:9:10];
        end
    initial
        begin
            $monitor ($time, " %d %b", DP.C, done);
        end
endmodule
```